



Faculty of Engineering & Technology
Electrical & Computer Engineering Department

ADVANCED DIGITAL SYSTEMS DESIGN
ENCS 3310

Project Report

Student's Name: Tariq Odeh

Student's No: 1190699

Sec: 2

Instructor: Dr. Abdallatif Abuissa

Date: 20th December 2021

Table of Contents

1. Introduction	1
2. Theoretical overview	1
2.1. Ripple Adder/Subtractor	1
2.2. Look-ahead Adder/Subtractor	2
2.3. Magnitude Comparator	2
3. Design philosophy	3
3.1. Basic Gates	3
3.2. Stage 1.....	3
3.3. Stage 2.....	4
3.4. Test Generator	5
3.5. Result Analyze.....	5
3.6. Verification Stage 1 & Stage 2.....	5
4. Simulation and results.....	6
4.1. Stage 1 with ripple adder/subtractor	6
4.2. Stage 2 with magnitude comparator	7
5. Conclusion and future works	8
6. References	9
7. Appendix	10
7.1. Code of Basic Gates.....	10
7.2. Code of half and full adder	13
7.3. Code of N-bit Ripple Adder/Subtractor	14
7.4. Code of N-bit Comparator.....	14
7.5. Code of Stage 1 with ripple adder/subtractor	15
7.6. Code of 1-Bit Magnitude comparator.....	15
7.7. Code of 4-Bit Magnitude comparator.....	15
7.8. Code of 8-Bit Magnitude comparator.....	16
7.8. Code of Stage 2 with Magnitude comparator	16
7.9. Circuit of 4-bit magnitude comparator	17
7.10. Code of Test Generator	18
7.11. Code of Result Analyze	18
7.12. Code of Verification Stage 1 & Stage 2.....	19
7.13. Full Code with comments	19

List Of Figures

Figure 1: Ripple Carry Adder/Subtractor.....	1
Figure 2: Carry Look-ahead adder	2
Figure 3: 1-Bit Magnitude Comparator	2
Figure 4: 8-Bit Comparator circuit.....	3
Figure 5: Stage 2 with Magnitude comparator	4
Figure 6: block diagram of the design	5
Figure 7: Stage 1 simulation when Clk = 133 ns	6
Figure 8: Stage 1 simulation when Clk less than 133 ns.....	6
Figure 9: Stage 2 simulation when Clk = 25 ns	7
Figure 10: Stage 2 simulation when Clk less than 25 ns.....	7

1. Introduction

In this project, we will implement an 8-bit Comparator for signed 2's complement representation numbers structurally by using several basic gates and entities with certain delays, in two stages. And then we want verification the two stages by creating a test generator that generates all correct possibilities for the device and compared them with the resulting values from stages. The first stage It will implement by using ripple adder-subtractor or look ahead and in second stage by using Magnitude comparator and the sign bit (we will talk about these circuits in general), We will calculate the duration of delay for each stage to use in testing the outputs.

Using the basic gates, we will build the important circuits that we will use in several stages, such as full adder, n-bit full adder. And we will focus on implementing these circuits in generic which take n-bit, in addition to focusing on building circuits with the least possible delay time through the use of NAND gates, and we will build circuits in several ways structurally, which makes this project more flexible and faster and the user can modify the design. Finally, we'll simulate the project and test all of the findings and outputs in both stages using (Aldec Active-HDL Student Edition).

2. Theoretical overview

2.1. Ripple Adder/Subtractor

A ripple adder-subtractor is a special type of circuit that is used to perform both operations addition and subtraction. The process to be used depends on the value of the control signal M. The ripple adder-subtractor is one of the most important components of the arithmetic logical unit, and it is called ripple carry because each carry bit is rippled to the next stage. The circuit consists of n full adders since we are performing operation on n-bit numbers.

As shown in the figure below, the first full adder has three input c_{in} , A_0 , and B_0 XOR M. and has two outputs S_0 and carry C_{out} . If the value of control line is $M = 1$, the output of $B_0 \text{ XOR } 1 = B_0'$, and the output of full adder is $S_0 = A_0 + B_0'$ and carry C_{out} , which is the 2's complement for two numbers A and B. This suggests that when $M=1$, the operation being performed on the four-bit numbers is subtraction.

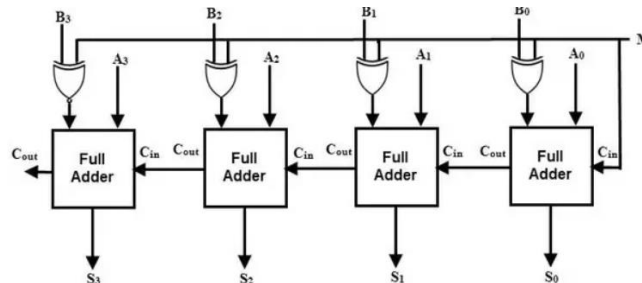


Figure 1: Ripple Carry Adder/Subtractor

2.2. Look-ahead Adder/Subtractor

Each adder block in a ripple adder-subtractor waits for the carry from the preceding block. As a result, unless the input carry is known, it is impossible to produce the sum and carry of any block. As a result, there will be a significant time delay due to carry propagation delay. The look-ahead adder/subtractor minimizes the propagation latency by using more complicated hardware, it is a faster parallel adder, but it is also more expensive. It takes use of the fact that each bit location in the addition may be used to determine whether a carry will be created at that bit or propagated via that bit.

 


Figure 2: Carry Look-ahead adder

2.3. Magnitude Comparator

A magnitude digital Comparator is a combinational circuit that compares two digital or binary numbers (say, A and B) to determine whether one is equal to, less than, or greater than the other. Digital or binary comparators are made up of standard AND, NOR, and NOT gates that compare digital signals at their input terminals and output a result dependent on the state of those inputs. Three binary variables show the outcome of the comparison: $A=B$, $A>B$, or $A<B$. Below is a block diagram of an n-bit comparator, which compares two n-bit integers and generates their relation between themselves.

 


Figure 3: 1-Bit Magnitude Comparator

3. Design philosophy

3.1. Basic Gates

To start building the stages, we need to implement the basic gates. As shown in appendix ([Code of basic gates](#)), we built the gates in generic (N-bit) with one PORT, and (2-bit) in two PORTS, which will make it easier to implement the stages and make the design more flexible.

3.2. Stage 1

- **Half and full adder**

We implemented half adder and the full adder to use later in building ripple full adder. As shown in appendix ([Code of half and full adder](#)), the full adder can be built in three ways: first by using AND gates, XOR gates and OR gates, second by using half adder and third by using NAND gate. We used NAND gates to decrease the time of delay.

- **N-bit Ripple Adder/Subtractor**

We used the full adder library to implement the code for n-bit Ripple Adder/Subtractor as shown in appendix ([Code of N-bit Ripple Adder/Subtractor](#)). In this design we can use it as adder by making $C_{in} = 0$ and we can use it as subtractor by making $C_{in} = 1$. In this stage we want to use the subtractor to find 2's complement of B, so we making $C_{in} = 1$. We tried to build Look-ahead Adder/Subtractor, as it is faster in performance, but we had difficulty building it properly structurally.

- **N-bit Comparator**

By using the n-bit ripple adder/subtractor library and the basic gates, we built n-Bit Comparator for signed 2's complement representation numbers, that use the output of n-bit ripple adder/subtractor (overflow, Cout, SUM, and the last bit of SUM) to determine the comparison output, as shown in appendix ([Code of N-bit Comparator](#)). In the figure below show the circuit which takes the output of n-bit ripple adder/subtractor and determines the result of the comparison.

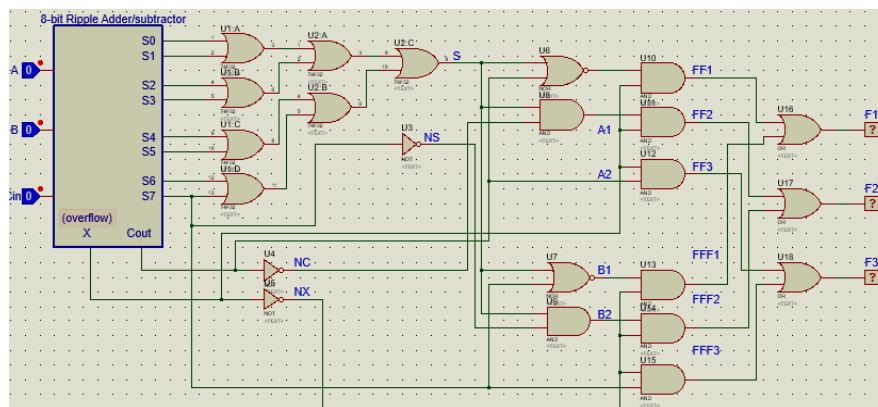


Figure 4: 8-Bit Comparator circuit

- **Stage 1 with ripple adder/subtractor**

Here we built the stage 1 by using n-Bit comparator library and making it 8-bit. From here we can easily modify the design for any number of bits we need, as shown in appendix ([Code of Stage 1 with ripple adder/subtractor](#)).

3.3. Stage 2

- **1-Bit Magnitude comparator**

We implemented 1-bit magnitude comparator by using basic gates to use later in building 4-bit magnitude comparator. As shown in appendix ([Code of 1-bit magnitude comparator](#)) the 1-bit magnitude comparator by using AND gates, XNOR gates and INVERTER gates.

- **4-Bit Magnitude comparator**

We implemented 4-bit magnitude comparator by using 1-bit magnitude comparator library and basic gates, to use later in building 8-bit magnitude comparator. As shown in appendix ([Code of 4-bit magnitude comparator](#)) we find the possibilities for greater, less and equal output using OR/AND gates, we can see the circuit in appendix ([7.9](#)).

- **8-Bit Magnitude comparator**

We implemented 8-bit magnitude comparator by using two of 4-bit magnitude comparator library and basic gates, to use later in building stage 2. As shown in appendix ([Code of 8-bit magnitude comparator](#)) we find the possibilities for greater, less and equal output using OR/AND gates.

- **Stage 2 with magnitude comparator**

We implemented stage 2 by using 8-bit magnitude comparator library and basic gates. As shown in appendix ([Code of Stage 2 with Magnitude comparator](#)), we used XOR gate to deal with sign bit and to find to output.

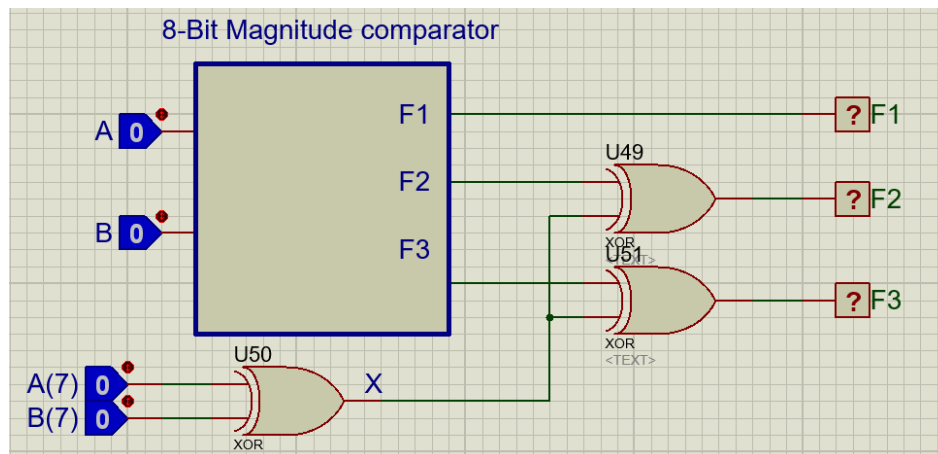


Figure 5: Stage 2 with Magnitude comparator

3.4. Test Generator

In this generator we made two nested loop to reach all possible values of A and B and passed to output when the clock input rises, and at each value of A and B will resulting the correct output in behavioral logic as shown in appendix ([Code of Test Generator](#)).

3.5. Result Analyze

The result analyzer makes sure that the output from our system equals the correct which we calculated in Test Generator when the clock input rises, and if not equals print an error by using assert component and report to typing the error message. As shown in appendix ([Code of Result Analyze](#)).

3.6. Verification Stage 1 & Stage 2

In verification we want to automatically decide if the design works by checks the answers for correctness and notifies the user of any error, so in verification we built the whole system with a test generator, result analyzer and the stage we want. The generator and analyzer will have the same clock signal, after a specified amount of time, the clock signal reverses, and the test generator alters the A and B signals, sending the right output to the result analyzer. The outputs A and B are sent to the system, which generates an output. This output is then sent to the result analyzer, which determines whether or not the output is valid based on the test generator's proper result. The figure below shown the block diagram for design and we can see the code in appendix ([Code of Verification Stage 1 & Stage 2](#)).

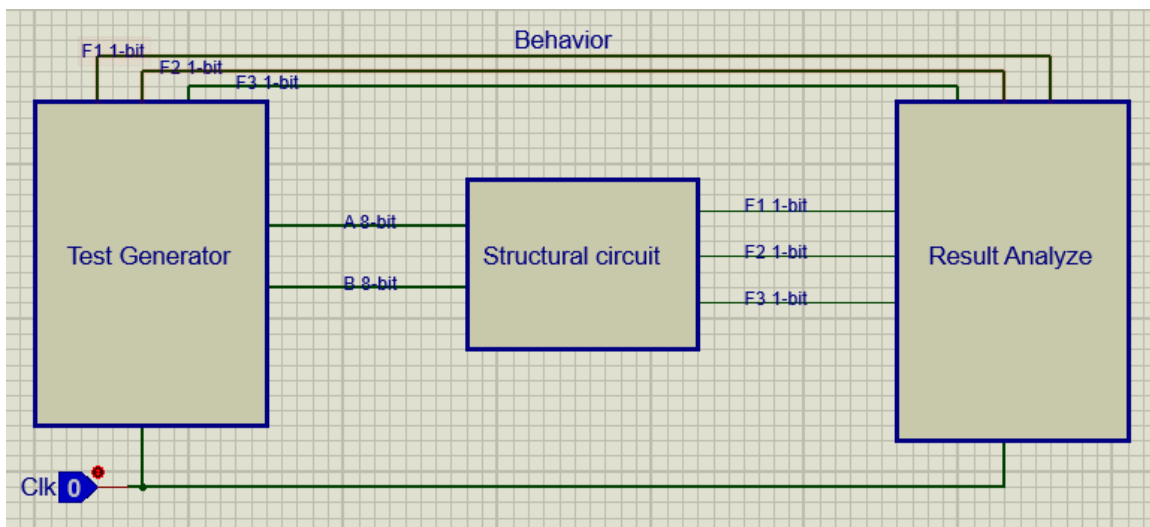


Figure 6: block diagram of the design

4. Simulation and results

The full Code with comments shown in appendix ([Full Code with comments](#)).

4.1. Stage 1 with ripple adder/subtractor

From the screenshots below for the simulation shows the results of the structurally circuit that we built and the results of test generator (behavioral), and shows the difference between the results. We can see that the results of the structurally circuit that we built have some glitches which we want to show to see the difference between the results, and through it, we can set the clock.

And based on simulation and the glitches that have appeared, we found that when the value of the **Clk = 133 ns**, we will get matched results without any errors, since if we take a lower value from it, an error will happen.



Figure 7: Stage 1 simulation when Clk = 133 ns

We notice in Figure 8, that we made Clk less than 133 ns, which showed some errors.

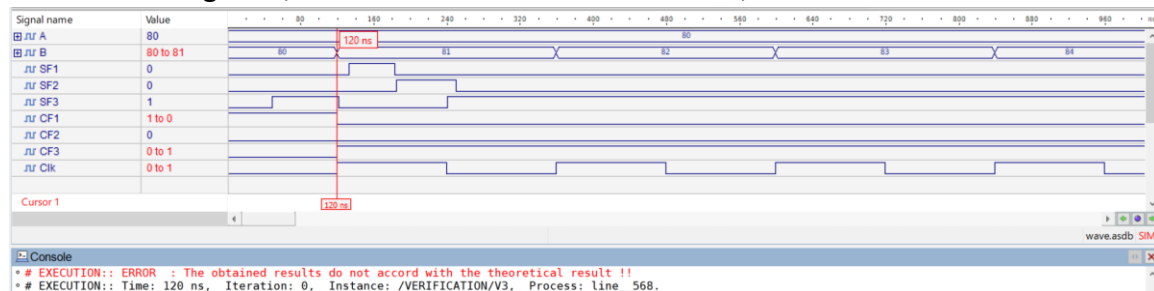


Figure 8: Stage 1 simulation when Clk less than 133 ns

4.2. Stage 2 with magnitude comparator

From the screenshots below for the simulation shows the results of the structurally circuit that we built and the results of test generator (behavioral), and shows the difference between the results. We can see that the results of the structurally circuit that we built have some glitches which we want to show to see the difference between the results, and through it, we can set the clock.

And based on simulation and the glitches that have appeared, we found that when the value of the **Clk = 25 ns**, we will get matched results without any errors, since if we take a lower value from it, an error will happen.

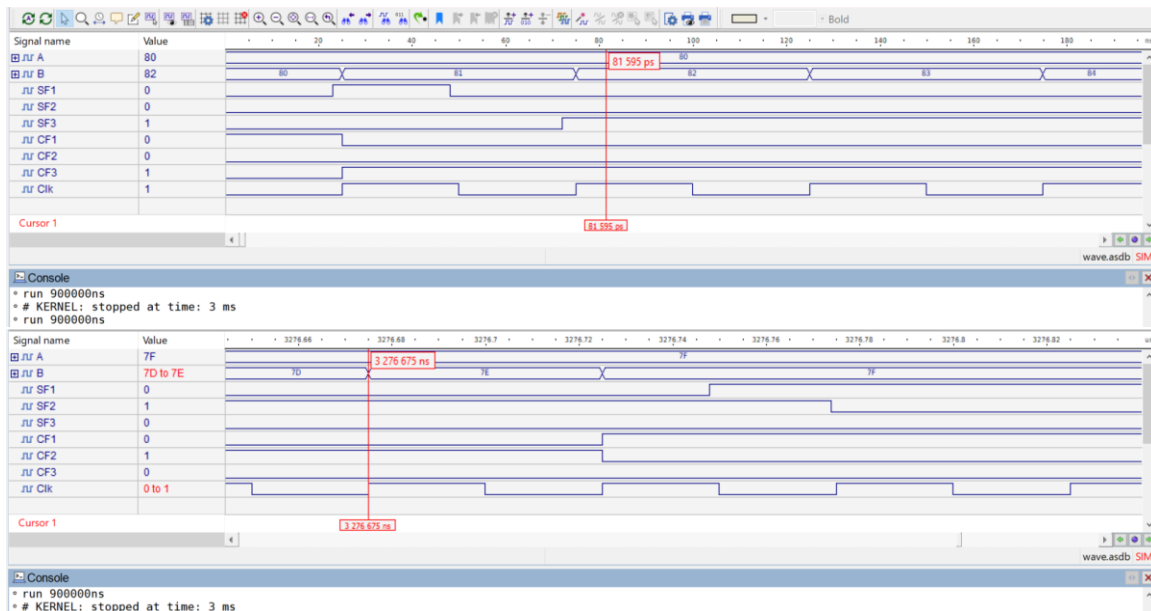


Figure 9: Stage 2 simulation when Clk = 25 ns

We notice in Figure 10, that we made Clk less than 25 ns, which showed some errors.

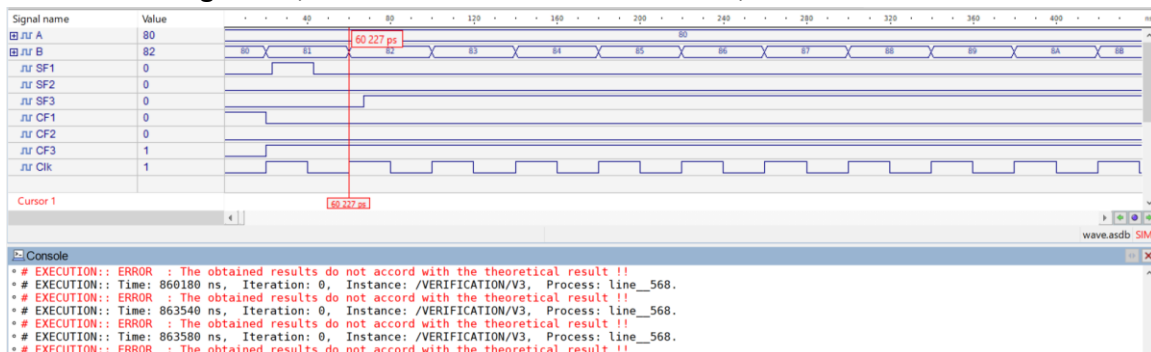


Figure 10: Stage 2 simulation when Clk less than 25 ns

5. Conclusion and future works

In conclusion, we built two stages structurally in this project and we successfully design an 8-bit Comparator for signed 2's complement and then write a functioning verification method. The results of the preceding methods agree with the theoretical outcomes, and we found that the built-in test is helpful in ensuring that the outputs are accurate. Furthermore, we infer that we can build large systems with smaller ones. We learned a lot about types of circuits like Ripple Adder/subtractor, Look-ahead Adder/subtractor, and magnitude (unsigned) comparator. And by creating entities in behavioral and structural logics, making a delay, testing the systems, and learning how to create commands like how to print an error, we grew more accustomed with VHDL.

During the project implementation process, our focus was on reaching the best possible design and the best performance. It was necessary to expand our knowledge and search for several topics and ways to improve performance and to facilitate our work and ensure access to a better design. On the design side, we focused on the clarity of the code, the clear structure, and the ability to modify the design, as most of the blocks were built in a general way, which facilitates the modification and development of the design, and in terms of performance, we tried to use the gates with the least delay time, such as NAND and NOR.

We faced many challenges and problems during the implementation of this project. We faced is how to build circuits in the general way, and also how to reach a correct design through which a correct output can be obtained. We had problems with how to build the lookahead carry structurally, so we tried over and over and finally had to use behavioral in the build so we worked on ripple adder/subtractor. Most of the challenges and problems were solved through research and experience.

In conclusion, it is necessary to look to the future of the project in order to be able to solve any defect that appears in the design and to ensure continuous development. We are looking forward to improving the delay time of the system by using the Look-ahead Adder/subtractor as it is faster in performance in addition to using gates with less delay time, and we will convert all the design to the general format to reach the high flexibility in the design. We will show our project to many experts to try and and we will take feedback and build on it to improve the design.

6. References

- [1] *4-bit binary adder-subtractor*. GeeksforGeeks. (2021, October 21). Retrieved December 19, 2021, from <https://www.geeksforgeeks.org/4-bit-binary-adder-subtractor/>
- [2] *Dynamic 16-bit carry- lookaheadadder/subtractor*. (2020, April 45). Retrieved December 19, 2021, from <http://people.ee.duke.edu/~jmorizio/ece261/F07/projects/CarryLookahead.pdf>
- [3] kishorekashyap. (2017, November 21). *Magnitude comparator 1 bit, 2 bit, 3 bit, 4 bit*. YouTube. Retrieved December 19, 2021, from <https://www.youtube.com/watch?v=7-MbS-wKWuw>
- [4] *Performance analysis of different bit carry look ahead ...* (2020, June 4). Retrieved December 19, 2021, from https://www.researchgate.net/publication/319236867_Performance_Analysis_of_Different_Bit_Carry_Look_Ahead_Adder_Using_VHDL_Environment
- [5] Sas, W. (2021, August 4). *Two's complement calculator*. Omni Calculator. Retrieved December 19, 2021, from <https://www.omnicalculator.com/math/twos-complement>
- [6] uxnzdwsiuxnzdwsi 122 bronze badges, Giorgi TsiklauriGiorgi Tsiklauri 7, John AspinallJohn Aspinall 933 bronze badges, mhawkemhawke 78.1k99 gold badges103103 silver badges133133 bronze badges, & WJSWJS 26.2k44 gold badges1919 silver badges3434 bronze badges. (1969, April 1). *Two's complement binary range for 8-bit*. Stack Overflow. Retrieved December 19, 2021, from <https://stackoverflow.com/questions/66538718/twos-complement-binary-range-for-8-bit>
- [7] YouTube. (2018, January 24). *Carry ripple adder and subtractor circuits*. YouTube. Retrieved December 19, 2021, from <https://www.youtube.com/watch?v=-21zUqEKeqk>

7. Appendix

7.1. Code of Basic Gates

```
12 -----
13 --                INVERTER GATE (1 PORT)                --
14 -----
15 LIBRARY IEEE;
16 USE IEEE.STD_LOGIC_1164.ALL;
17
18 ENTITY NOT_1P IS
19     PORT(A: IN STD_LOGIC:= '0';      --1 bit Input
20           F: OUT STD_LOGIC:= '0');    --1 bit Output
21 END ENTITY NOT_1P;
22
23 ARCHITECTURE STRUCT_NOT_1P OF NOT_1P IS
24 BEGIN
25     F <= NOT A AFTER 2 NS;            --2 ns delay
26 END ARCHITECTURE STRUCT_NOT_1P;
27
28
29 -----
30 --                NAND GATE (N-BIT)                      --
31 -----
32 LIBRARY IEEE;
33 USE IEEE.STD_LOGIC_1164.ALL;
34
35 ENTITY NAND_NBIT IS
36     GENERIC ( N : POSITIVE := 2);    --N bit Input
37     PORT(A: IN STD_LOGIC_VECTOR (N-1 DOWNTO 0):= "00000000";
38           F: OUT STD_LOGIC:= '0');    --1 bit Output
39 END ENTITY NAND_NBIT;
40
41 ARCHITECTURE STRUCT_NAND_NBIT OF NAND_NBIT IS
42 SIGNAL TEMP : STD_LOGIC_VECTOR (N-1 DOWNTO 0);
43 BEGIN
44     TEMP(0) <= A(0);
45     FLOOP: FOR i IN 1 TO (N-1) GENERATE
46         TEMP(i) <= TEMP(i-1) AND A(i);
47     END GENERATE FLOOP;
48     F <= NOT(TEMP(N-1)) AFTER 5 NS;    --NAND = NOT(AND)
49 END ARCHITECTURE STRUCT_NAND_NBIT;    --5 ns delay
50
51
52 -----
53 --                NAND GATE (2 PORTS)                    --
54 -----
55 LIBRARY IEEE;
56 USE IEEE.STD_LOGIC_1164.ALL;
57
58 ENTITY NAND_2P IS
59     PORT(A,B: IN STD_LOGIC:= '0';    --2 bit Input
60           F: OUT STD_LOGIC:= '0');    --1 bit Output
61 END ENTITY NAND_2P;
62
63 ARCHITECTURE STRUCT_NAND_2P OF NAND_2P IS
64 BEGIN
65     F <= A NAND B AFTER 5 NS;          --5 ns delay
66     -- F <= NOT(A AND B) AFTER 5 NS;
67 END ARCHITECTURE STRUCT_NAND_2P;
68
69
70 -----
71 --                NOR GATE (N-BIT)                      --
72 -----
73 LIBRARY IEEE;
74 USE IEEE.STD_LOGIC_1164.ALL;
75
76 ENTITY NOR_NBIT IS
77     GENERIC ( N : POSITIVE := 2);    --N bit Input
78     PORT(A: IN STD_LOGIC_VECTOR (N-1 DOWNTO 0):= "00000000";
79           F: OUT STD_LOGIC:= '0');    --1 bit Output
80 END ENTITY NOR_NBIT;
81
82 ARCHITECTURE STRUCT_NOR_NBIT OF NOR_NBIT IS
83 SIGNAL TEMP : STD_LOGIC_VECTOR (N-1 DOWNTO 0);
84 BEGIN
85     TEMP(0) <= A(0);
86     FLOOP: FOR i IN 1 TO (N-1) GENERATE
87         TEMP(i) <= TEMP(i-1) OR A(i);
88     END GENERATE FLOOP;
89     F <= NOT(TEMP(N-1)) AFTER 5 NS;    --NOR = NOT(OR)
90 END ARCHITECTURE STRUCT_NOR_NBIT;    --5 ns delay
91
92
```

```

93 -----
94 -- NOR GATE (2 PORTS) --
95 -----
96 LIBRARY IEEE;
97 USE IEEE.STD_LOGIC_1164.ALL;
98
99 ENTITY NOR_2P IS
100     PORT(A,B: IN STD_LOGIC:= '0'; --2 bit Input
101           F: OUT STD_LOGIC:= '0'); --1 bit Output
102 END ENTITY NOR_2P;
103
104 ARCHITECTURE STRUCT_NOR_2P OF NOR_2P IS
105     BEGIN
106         F <= A NOR B AFTER 5 NS; --5 ns delay
107         -- F <= NOT(A OR B) AFTER 5 NS;
108     END ARCHITECTURE STRUCT_NOR_2P;
109
110 -----
111 -- AND GATE (N-BIT) --
112 -----
113
114 LIBRARY IEEE;
115 USE IEEE.STD_LOGIC_1164.ALL;
116
117 ENTITY AND_NBIT IS
118     GENERIC ( N : POSITIVE := 2); --N bit Input
119     PORT(A: IN STD_LOGIC_VECTOR (N-1 DOWNTO 0):= "00000000";
120           F: OUT STD_LOGIC:= '0'); --1 bit Output
121 END ENTITY AND_NBIT;
122
123 ARCHITECTURE STRUCT_AND_NBIT OF AND_NBIT IS
124     SIGNAL TEMP : STD_LOGIC_VECTOR (N-1 DOWNTO 0);
125     BEGIN
126         TEMP(0) <= A(0);
127         FLOOP: FOR i IN 1 TO (N-1) GENERATE
128             TEMP(i) <= TEMP(i-1) AND A(i);
129         END GENERATE FLOOP;
130         F <= TEMP(N-1) AFTER 7 NS; --7 ns delay
131     END ARCHITECTURE STRUCT_AND_NBIT;
132
133 -----
134 -- AND GATE (2 PORTS) --
135 -----
136
137 LIBRARY IEEE;
138 USE IEEE.STD_LOGIC_1164.ALL;
139
140 ENTITY AND_2P IS
141     PORT(A,B: IN STD_LOGIC:= '0'; --2 bit Input
142           F: OUT STD_LOGIC:= '0'); --1 bit Output
143 END ENTITY AND_2P;
144
145 ARCHITECTURE STRUCT_AND_2P OF AND_2P IS
146     BEGIN
147         F <= A AND B AFTER 7 NS; --7 ns delay
148     END ARCHITECTURE STRUCT_AND_2P;
149
150 -----
151 -- OR GATE (N-BIT) --
152 -----
153
154 LIBRARY IEEE;
155 USE IEEE.STD_LOGIC_1164.ALL;
156
157 ENTITY OR_NBIT IS
158     GENERIC ( N : POSITIVE := 2); --N bit Input
159     PORT(A: IN STD_LOGIC_VECTOR (N-1 DOWNTO 0):= "00000000";
160           F: OUT STD_LOGIC:= '0'); --1 bit Output
161 END ENTITY OR_NBIT;
162
163 ARCHITECTURE STRUCT_OR_NBIT OF OR_NBIT IS
164     SIGNAL TEMP : STD_LOGIC_VECTOR (N-1 DOWNTO 0);
165     BEGIN
166         TEMP(0) <= A(0);
167         FLOOP: FOR i IN 1 TO (N-1) GENERATE
168             TEMP(i) <= TEMP(i-1) OR A(i);
169         END GENERATE FLOOP;
170         F <= TEMP(N-1) AFTER 7 NS; --7 ns delay
171     END ARCHITECTURE STRUCT_OR_NBIT;

```

```

172 -----
173 -- OR GATE (2 PORTS) --
174 -----
175 LIBRARY IEEE;
176 USE IEEE.STD_LOGIC_1164.ALL;
177
178 ENTITY OR_2P IS
179     PORT(A,B: IN STD_LOGIC:= '0'; --2 bit Input
180          F: OUT STD_LOGIC:= '0'); --1 bit Output
181 END ENTITY OR_2P;
182
183 ARCHITECTURE STRUCT_OR_2P OF OR_2P IS
184     BEGIN
185         F <= A OR B AFTER 7 NS; --7 ns delay
186 END ARCHITECTURE STRUCT_OR_2P;
187
188
189 -----
190 -- XNOR GATE (2 PORTS) --
191 -----
192 LIBRARY IEEE;
193 USE IEEE.STD_LOGIC_1164.ALL;
194
195 ENTITY XNOR_2P IS
196     PORT(A,B: IN STD_LOGIC:= '0'; --2 bit Input
197          F: OUT STD_LOGIC:= '0'); --1 bit Output
198 END ENTITY XNOR_2P;
199
200 ARCHITECTURE STRUCT_XNOR_2P OF XNOR_2P IS
201     BEGIN
202         F <= A XNOR B AFTER 9 NS; --9 ns delay
203 END ARCHITECTURE STRUCT_XNOR_2P;
204
205
206 -----
207 -- XOR GATE (2 PORTS) --
208 -----
209 LIBRARY IEEE;
210 USE IEEE.STD_LOGIC_1164.ALL;
211
212 ENTITY XOR_2P IS
213     PORT(A,B: IN STD_LOGIC:= '0'; --2 bit Input
214          F: OUT STD_LOGIC:= '0'); --1 bit Output
215 END ENTITY XOR_2P;
216
217 ARCHITECTURE STRUCT_XOR_2P OF XOR_2P IS
218     BEGIN
219         F <= A XOR B AFTER 12 NS; --12 ns delay
220 END ARCHITECTURE STRUCT_XOR_2P;
221
222

```

7.2. Code of half and full adder

```
223 -----
224 -- Half Adder --
225 -----
226 LIBRARY IEEE;
227 USE IEEE.STD_LOGIC_1164.ALL;
228
229 ENTITY HA IS
230     PORT(A,B: IN STD_LOGIC:= '0';           --Input
231           Sum,Cout: OUT STD_LOGIC:= '0');    --Output
232 END ENTITY HA;
233
234 ARCHITECTURE STRUCT_HA OF HA IS
235     SIGNAL X : STD_LOGIC_VECTOR (1 DOWNTO 0):= "00";
236     BEGIN
237         X <= A & B;
238         H1: ENTITY WORK.XOR_2P(STRUCT_XOR_2P) PORT MAP (A,B,Sum);           --Sum = A XOR B
239         H2: ENTITY WORK.AND_NBIT(STRUCT_AND_NBIT) GENERIC MAP(2) PORT MAP (X,Cout);    --Cout = A AND B
240     END ARCHITECTURE STRUCT_HA;
241
242
243 -----
244 -- Full Adder --
245 -----
246 LIBRARY IEEE;
247 USE IEEE.STD_LOGIC_1164.ALL;
248
249 ENTITY FAD IS
250     PORT(A,B,Cin: IN STD_LOGIC:= '0';
251           Sum,Cout: OUT STD_LOGIC:= '0');
252 END ENTITY FAD;
253
254 ARCHITECTURE STRUCT_FAD OF FAD IS
255     SIGNAL N1,N2,N3,N4,N5,N6,N7: STD_LOGIC := '0';
256     BEGIN
257         --First way to implement Full Adder Using XOR,AND,OR gates
258         --F1: ENTITY WORK.XOR_2P(STRUCT_XOR_2P) PORT MAP(A,B,N1);           --SUM = A XOR B XOR Cin
259         --F2: ENTITY WORK.XOR_2P(STRUCT_XOR_2P) PORT MAP(N1,Cin,Sum);       --Cout = Cin.(A XOR B) + A.B
260         --F3: ENTITY WORK.AND_2P(STRUCT_AND_2P) PORT MAP(A,B,N2);
261         --F4: ENTITY WORK.AND_2P(STRUCT_AND_2P) PORT MAP(N1,Cin,N3);
262         --F5: ENTITY WORK.OR_2P(STRUCT_OR_2P) PORT MAP(N2,N3,Cout);
263
264         --Second way to implement Full Adder Using Half Adder
265         --F1: ENTITY WORK.HA(STRUCT_HA) PORT MAP(A,B,N1,N2);
266         --F2: ENTITY WORK.HA(STRUCT_HA) PORT MAP(N1,Cin,Sum,N3);
267         --F3: ENTITY WORK.OR_2P(STRUCT_OR_2P) PORT MAP(N2,N3,Cout);
268
269         --Third way to implement Full Adder Using NAND gate (faster)
270         F1: ENTITY WORK.NAND_2P(STRUCT_NAND_2P) PORT MAP(A,B,N1);
271         F2: ENTITY WORK.NAND_2P(STRUCT_NAND_2P) PORT MAP(N1,A,N2);
272         F3: ENTITY WORK.NAND_2P(STRUCT_NAND_2P) PORT MAP(N1,B,N3);
273         F4: ENTITY WORK.NAND_2P(STRUCT_NAND_2P) PORT MAP(N2,N3,N4);
274         F5: ENTITY WORK.NAND_2P(STRUCT_NAND_2P) PORT MAP(N4,Cin,N5);
275         F6: ENTITY WORK.NAND_2P(STRUCT_NAND_2P) PORT MAP(N5,N1,Cout);
276         F7: ENTITY WORK.NAND_2P(STRUCT_NAND_2P) PORT MAP(N5,Cin,N6);
277         F8: ENTITY WORK.NAND_2P(STRUCT_NAND_2P) PORT MAP(N5,N4,N7);
278         F9: ENTITY WORK.NAND_2P(STRUCT_NAND_2P) PORT MAP(N6,N7,Sum);
279     END ARCHITECTURE STRUCT_FAD;
280
281 -----
```


7.3. Code of N-bit Ripple Adder/Subtractor

```

282 -----
283 --          n-Bit Ripple Adder/subtractor          --
284 -----
285 LIBRARY IEEE;
286 USE IEEE.STD_LOGIC_1164.ALL;
287
288 ENTITY NBIT_ADDER IS
289     GENERIC ( N : POSITIVE := 8);
290     PORT(A,B: IN STD_LOGIC_VECTOR (N-1 DOWNT0 0):= "00000000";
291           Cin: IN STD_LOGIC := '1';           --Set Cin = 1 to find 2's complement for B
292           Sum: OUT STD_LOGIC_VECTOR(N-1 DOWNT0 0):= "00000000";
293           Cout, OV: OUT STD_LOGIC:= '0');      --OV (overflow)
294 END ENTITY NBIT_ADDER;
295
296 ARCHITECTURE STRUCT_RIPPLE OF NBIT_ADDER IS
297     SIGNAL CARRY : STD_LOGIC_VECTOR (N DOWNT0 0):= "000000000";
298     SIGNAL X :STD_LOGIC_VECTOR (N-1 DOWNT0 0):= "00000000"; --to save 2's complement of B
299 BEGIN
300     CARRY(0) <= Cin;
301     Cout <= CARRY(N);
302     R1: ENTITY WORK.XOR_2P(STRUCT_XOR_2P) PORT MAP (CARRY(N),CARRY(N-1),OV);
303     FLOOP: FOR i IN 0 TO (N-1) GENERATE           --Loop to generate ripple Adder/subtractor
304         R2: ENTITY WORK.XOR_2P(STRUCT_XOR_2P) PORT MAP (B(i),Cin,X(i)); --if Cin = 0 then ripple Adder work, if Cin = 1 ripple subtractor work
305         R3: ENTITY WORK.FAD(STRUCT_FAD) PORT MAP (A(i),X(i),CARRY(i),Sum(i),CARRY(i+1));
306     END GENERATE FLOOP;
307 END ARCHITECTURE STRUCT_RIPPLE;
308

```

7.4. Code of N-bit Comparator

```

309 -----
310 ----          n-Bit Comparator          ----
311 -----
312 LIBRARY IEEE;
313 USE IEEE.STD_LOGIC_1164.ALL;
314
315 ENTITY NBIT_COMPARATOR IS
316     GENERIC ( N : POSITIVE := 8);
317     PORT(A,B: IN STD_LOGIC_VECTOR (N-1 DOWNT0 0):= "00000000"; --Input
318           F1,F2,F3: OUT STD_LOGIC:= '0');           --Output: F1(A=B), F2(A>B), and F3 (A<B).
319 END ENTITY NBIT_COMPARATOR;
320
321 ARCHITECTURE STRUCT_NBIT_COMPARATOR OF NBIT_COMPARATOR IS
322     SIGNAL SUM : STD_LOGIC_VECTOR (N-1 DOWNT0 0):= "00000000";
323     SIGNAL Cout,X,S : STD_LOGIC:= '0';           --X to check overflow, S to check if sum equal zero
324     SIGNAL NC,NS,NX: STD_LOGIC:= '0';           --NC (not Cout), NS (not S(N-1)), NX (not Overflow)
325     SIGNAL FF1,FF2,FF3: STD_LOGIC:= '0';         --to save output of F1,F2,F3 if there is overflow
326     SIGNAL FFF1,FFF2,FFF3: STD_LOGIC:= '0';      --to save output of F1,F2,F3 if there is not overflow
327     SIGNAL A1,A2,B1,B2: STD_LOGIC:= '0';
328
329 BEGIN
330     P1: ENTITY WORK.NBIT_ADDER(STRUCT_RIPPLE) GENERIC MAP(N) PORT MAP(A,B,'1',SUM,Cout,X); --ripple subtractor (the output of overflow save in X)
331     P3: ENTITY WORK.OR_NBIT(STRUCT_OR_NBIT) GENERIC MAP(N) PORT MAP(SUM,S);           --check if sum equal zero
332     P4: ENTITY WORK.NOT_1P(STRUCT_NOT_1P)PORT MAP(Cout,NC);           --NC (not Cout)
333     P5: ENTITY WORK.NOT_1P(STRUCT_NOT_1P)PORT MAP(SUM(N-1),NS);       --NS (not S(N-1))
334     P6: ENTITY WORK.NOT_1P(STRUCT_NOT_1P)PORT MAP(X,NX);           --NX (not Overflow)
335
336     X1: ENTITY WORK.NOR_2P(STRUCT_NOR_2P) PORT MAP (Cout,S,A1);       --find the value of F1,F2,F3 if there is overflow
337     X2: ENTITY WORK.AND_2P(STRUCT_AND_2P) PORT MAP (NC,S,A2);
338     X3: ENTITY WORK.AND_2P(STRUCT_AND_2P) PORT MAP (X,A1,FF1);
339     X4: ENTITY WORK.AND_2P(STRUCT_AND_2P) PORT MAP (X,A2,FF2);
340     X5: ENTITY WORK.AND_2P(STRUCT_AND_2P) PORT MAP (X,Cout,FF3);
341
342     Y1: ENTITY WORK.NOR_2P(STRUCT_NOR_2P) PORT MAP (SUM(N-1),S,B1);   --find the value of F1,F2,F3 if there is not overflow
343     Y2: ENTITY WORK.AND_2P(STRUCT_AND_2P) PORT MAP (NS,S,B2);
344     Y3: ENTITY WORK.AND_2P(STRUCT_AND_2P) PORT MAP (NX,B1,FFF1);
345     Y4: ENTITY WORK.AND_2P(STRUCT_AND_2P) PORT MAP (NX,B2,FFF2);
346     Y5: ENTITY WORK.AND_2P(STRUCT_AND_2P) PORT MAP (NX,SUM(N-1),FFF3);
347
348     Z1: ENTITY WORK.OR_2P(STRUCT_OR_2P) PORT MAP(FF1,FFF1,F1);         --final value of F1,F2,F3
349     Z2: ENTITY WORK.OR_2P(STRUCT_OR_2P) PORT MAP(FF2,FFF2,F2);
350     Z3: ENTITY WORK.OR_2P(STRUCT_OR_2P) PORT MAP(FF3,FFF3,F3);
351
352 END ARCHITECTURE STRUCT_NBIT_COMPARATOR;
353

```

7.5. Code of Stage 1 with ripple adder/subtractor

```
354
355
356 -----
357      Stage_1 with ripple adder/subtractor      --
358 -----
359 LIBRARY IEEE;
360 USE IEEE.STD_LOGIC_1164.ALL;
361
362 ENTITY STAGE_1 IS
363     PORT(A,B: IN STD_LOGIC_VECTOR (7 DOWNTO 0)):= "00000000";    --8-bit input
364     F1,F2,F3: OUT STD_LOGIC:='0');    --Output: F1(A=B), F2(A>B), and F3 (A<B).
365 END ENTITY STAGE_1;
366
367 ARCHITECTURE STRUCT_STAGE_1 OF STAGE_1 IS
368     BEGIN
369         S1: ENTITY WORK.NBIT_COMPARATOR(STRUCT_NBIT_COMPARATOR) GENERIC MAP(8) PORT MAP(A,B,F1,F2,F3);
370     END ARCHITECTURE STRUCT_STAGE_1;
```

7.6. Code of 1-Bit Magnitude comparator

```
376 -----
377      1-Bit Magnitude comparator      --
378 -----
379 LIBRARY IEEE;
380 USE IEEE.STD_LOGIC_1164.ALL;
381
382 ENTITY MAGNCOMP_1BIT IS
383     PORT(A,B: IN STD_LOGIC:= '0');    --1-Bit input
384     F1,F2,F3: OUT STD_LOGIC:= '0');    --Output: F1(A=B), F2(A>B), and F3 (A<B)
385 END ENTITY MAGNCOMP_1BIT;
386
387 ARCHITECTURE STRUCT_MAGNCOMP_1BIT OF MAGNCOMP_1BIT IS
388     SIGNAL NA,NB : STD_LOGIC:= '0';    --NA(not A) , NB(not B)
389     BEGIN
390         M1: ENTITY WORK.XNOR_2P(STRUCT_XNOR_2P)PORT MAP(A,B,F1);
391         M2: ENTITY WORK.NOT_1P(STRUCT_NOT_1P)PORT MAP(B,NB);
392         M3: ENTITY WORK.AND_2P(STRUCT_AND_2P)PORT MAP(A,NB,F2);
393         M4: ENTITY WORK.NOT_1P(STRUCT_NOT_1P)PORT MAP(A,NA);
394         M5: ENTITY WORK.AND_2P(STRUCT_AND_2P)PORT MAP(NA,B,F3);
395     END ARCHITECTURE STRUCT_MAGNCOMP_1BIT;
```

7.7. Code of 4-Bit Magnitude comparator

```
398 -----
399      4-Bit Magnitude comparator      --
400 -----
401 LIBRARY IEEE;
402 USE IEEE.STD_LOGIC_1164.ALL;
403
404 ENTITY MAGNCOMP_4BIT IS
405     PORT(A,B: IN STD_LOGIC_VECTOR (3 DOWNTO 0)):= "0000";    --4-Bit input
406     F1,F2,F3: OUT STD_LOGIC:= '0');    --Output: F1(A=B), F2(A>B), and F3 (A<B).
407 END ENTITY MAGNCOMP_4BIT;
408
409 ARCHITECTURE STRUCT_MAGNCOMP_4BIT OF MAGNCOMP_4BIT IS
410     SIGNAL E,G,L :STD_LOGIC_VECTOR (3 DOWNTO 0):= "0000";    --E(equal)A=B, G(greater)A>B, L(less)A<B
411     SIGNAL GT,LT :STD_LOGIC_VECTOR (3 DOWNTO 0):= "0000";
412     SIGNAL LL1,GG1 :STD_LOGIC_VECTOR (1 DOWNTO 0):= "00";
413     SIGNAL LL2,GG2 :STD_LOGIC_VECTOR (2 DOWNTO 0):= "000";
414     SIGNAL LL3,GG3 :STD_LOGIC_VECTOR (3 DOWNTO 0):= "0000";
415     SIGNAL X1,X2,X3,X4,X5,X6 :STD_LOGIC := '0';
416     BEGIN
417         FLOOP1: FOR i IN 0 TO (3) GENERATE    --loop to compare 4 bit by using 1-Bit Magnitude comparator
418             M1: ENTITY WORK.MAGNCOMP_1BIT(STRUCT_MAGNCOMP_1BIT) PORT MAP (A(i),B(i),E(i),G(i),L(i));
419         END GENERATE FLOOP1;
420
421         LL1 <= L(2)&E(3);    --To find out the possibilities for greater or less
422         GG1 <= G(2)&E(3);
423         LL2 <= L(1)&E(3)&E(2);
424         GG2 <= G(1)&E(3)&E(2);
425         LL3 <= L(0)&E(3)&E(2)&E(1);
426         GG3 <= G(0)&E(3)&E(2)&E(1);
427
428         M2: ENTITY WORK.AND_NBIT(STRUCT_AND_NBIT) GENERIC MAP(2) PORT MAP(LL1,X1);
429         M3: ENTITY WORK.AND_NBIT(STRUCT_AND_NBIT) GENERIC MAP(2) PORT MAP(GG1,X2);
430         M4: ENTITY WORK.AND_NBIT(STRUCT_AND_NBIT) GENERIC MAP(3) PORT MAP(LL2,X3);
431         M5: ENTITY WORK.AND_NBIT(STRUCT_AND_NBIT) GENERIC MAP(3) PORT MAP(GG2,X4);
432         M6: ENTITY WORK.AND_NBIT(STRUCT_AND_NBIT) GENERIC MAP(4) PORT MAP(LL3,X5);
433         M7: ENTITY WORK.AND_NBIT(STRUCT_AND_NBIT) GENERIC MAP(4) PORT MAP(GG3,X6);
434
435         GT <= G(3)&X2&X4&X6;    --to check if greater or less
436         LT <= L(3)&X1&X3&X5;
437
438         M8: ENTITY WORK.AND_NBIT(STRUCT_AND_NBIT) GENERIC MAP(4) PORT MAP(E,F1);
439         M9: ENTITY WORK.OR_NBIT(STRUCT_OR_NBIT) GENERIC MAP(4) PORT MAP(GT,F2);
440         M10: ENTITY WORK.OR_NBIT(STRUCT_OR_NBIT) GENERIC MAP(4) PORT MAP(LT,F3);
441     END ARCHITECTURE STRUCT_MAGNCOMP_4BIT;
```


7.8. Code of 8-Bit Magnitude comparator

```
444 -----
445 --      8-Bit Magnitude comparator      --
446 -----
447 LIBRARY IEEE;
448 USE IEEE.STD_LOGIC_1164.ALL;
449
450 ENTITY MAGNCOMP_8BIT IS
451     PORT(A,B: IN STD_LOGIC_VECTOR (7 DOWNTO 0)):= "00000000";    --8-Bit input
452           F1,F2,F3: OUT STD_LOGIC:= '0';                          --Output: F1(A=B), F2(A>B), and F3 (A<B).
453 END ENTITY MAGNCOMP_8BIT;
454
455 ARCHITECTURE STRUCT_MAGNCOMP_8BIT OF MAGNCOMP_8BIT IS
456     SIGNAL T1,T2,T3,T4 :STD_LOGIC_VECTOR (3 DOWNTO 0):= "0000"; --To save A and B
457     SIGNAL E1,G1,L1 :STD_LOGIC:= '0';    --To save the output of the first 4-Bit Magnitude comparator
458     SIGNAL E2,G2,L2 :STD_LOGIC:= '0';    --To save the output of the second 4-Bit Magnitude comparator
459     SIGNAL GG,LL :STD_LOGIC:= '0';
460
461     BEGIN
462         T1 <= A(3)&A(2)&A(1)&A(0);
463         T2 <= B(3)&B(2)&B(1)&B(0);
464         T3 <= A(7)&A(6)&A(5)&A(4);
465         T4 <= B(7)&B(6)&B(5)&B(4);
466
467         M1: ENTITY WORK.MAGNCOMP_4BIT(STRUCT_MAGNCOMP_4BIT) PORT MAP (T1,T2,E1,G1,L1);
468         M2: ENTITY WORK.MAGNCOMP_4BIT(STRUCT_MAGNCOMP_4BIT) PORT MAP (T3,T4,E2,G2,L2);
469         M3: ENTITY WORK.AND_2P(STRUCT_AND_2P)PORT MAP(E2,G1,GG);    --To find out the possibilities for greater or less
470         M4: ENTITY WORK.AND_2P(STRUCT_AND_2P)PORT MAP(E2,L1,LL);
471
472         M5: ENTITY WORK.AND_2P(STRUCT_AND_2P)PORT MAP(E1,E2,F1);
473         M6: ENTITY WORK.OR_2P(STRUCT_OR_2P)PORT MAP(G2,GG,F2);
474         M7: ENTITY WORK.OR_2P(STRUCT_OR_2P)PORT MAP(L2,LL,F3);
475     END ARCHITECTURE STRUCT_MAGNCOMP_8BIT;
476
```

7.8. Code of Stage 2 with Magnitude comparator

```
478 -----
479 ----      Stage_2 with Magnitude comparator      --
480 -----
481 LIBRARY IEEE;
482 USE IEEE.STD_LOGIC_1164.ALL;
483
484 ENTITY STAGE_2 IS
485     PORT(A,B: IN STD_LOGIC_VECTOR (7 DOWNTO 0)):= "00000000";    --8-bit input
486           F1,F2,F3: OUT STD_LOGIC:= '0';                          --Output: F1(A=B), F2(A>B), and F3 (A<B).
487 END ENTITY STAGE_2;
488
489 ARCHITECTURE STRUCT_STAGE_2 OF STAGE_2 IS
490     SIGNAL X, FF2,FF3 : STD_LOGIC:= '0';
491     BEGIN
492
493         S1: ENTITY WORK.MAGNCOMP_8BIT(STRUCT_MAGNCOMP_8BIT) PORT MAP(A,B,F1,FF2,FF3);
494         S2: ENTITY WORK.XOR_2P(STRUCT_XOR_2P)PORT MAP(A(7),B(7),X);    --To check sign bit
495         S3: ENTITY WORK.XOR_2P(STRUCT_XOR_2P)PORT MAP(X,FF2,F2);    --To get a correct answer
496         S4: ENTITY WORK.XOR_2P(STRUCT_XOR_2P)PORT MAP(X,FF3,F3);
497
498     END ARCHITECTURE STRUCT_STAGE_2;
499
```

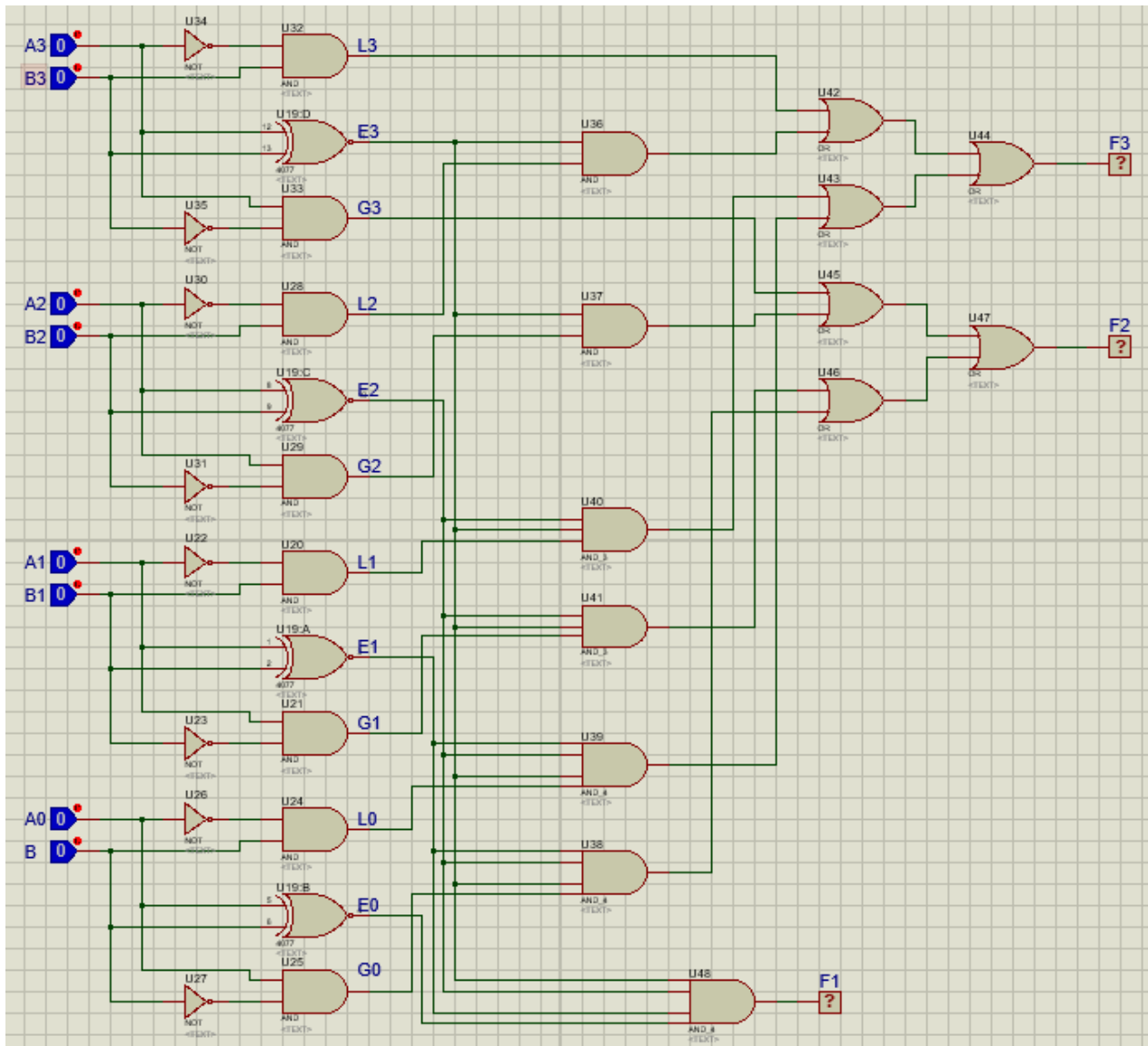7.9. Circuit of 4-bit magnitude comparator



7.10. Code of Test Generator

```
503 -----
504 ----- Test Generator -----
505 -----
506 LIBRARY IEEE;
507 USE IEEE.STD_LOGIC_1164.ALL;
508 USE IEEE.STD_LOGIC_SIGNED.ALL;
509 USE IEEE.STD_LOGIC_ARITH.ALL;
510
511 ENTITY TEST_GENERATOR IS
512     PORT(Clk: IN STD_LOGIC:= '0'; --clock input
513           A,B: OUT STD_LOGIC_VECTOR(7 DOWNTO 0):= "00000000"; --8 bit output:
514           F1,F2,F3: OUT STD_LOGIC:= '0'); --Output: F1(A=B), F2(A>B), and F3 (A<B)
515 END ENTITY TEST_GENERATOR;
516
517 ARCHITECTURE BEH_TEST_GENERATOR OF TEST_GENERATOR IS
518     SIGNAL IN1,IN2: STD_LOGIC_VECTOR(7 DOWNTO 0):= "00000000";
519 BEGIN
520     A <= IN1; --set the value of IN1 in A to send it to comparator
521     B <= IN2; --set the value of IN2 in B to send it to comparator
522     PROCESS --changes the values of IN1 and IN2 also (A and B) when the clock positive edge
523     BEGIN
524         FOR i IN -128 TO 127 LOOP --to go through all possible values
525             FOR j IN -128 TO 127 LOOP
526                 IN1(7 DOWNTO 0) <= CONV_STD_LOGIC_VECTOR(i,8); --conv from integer to STD_LOGIC
527                 IN2(7 DOWNTO 0) <= CONV_STD_LOGIC_VECTOR(j,8); --conv from integer to STD_LOGIC
528                 WAIT UNTIL rising_edge(Clk);
529             END LOOP;
530         END LOOP;
531         WAIT;
532     END PROCESS;
533
534     PROCESS (IN1,IN2) --implement the system using behavioural logic
535     BEGIN
536         IF (IN1 > IN2) THEN
537             F1 <= '0';
538             F2 <= '1';
539             F3 <= '0';
540         ELSIF (IN1 < IN2) THEN
541             F1 <= '0';
542             F2 <= '0';
543             F3 <= '1';
544         ELSE
545             F1 <= '1';
546             F2 <= '0';
547             F3 <= '0';
548         END IF;
549     END PROCESS;
550 END ARCHITECTURE BEH_TEST_GENERATOR;
```

7.11. Code of Result Analyze

```
553 -----
554 ----- Analyze -----
555 -----
556 LIBRARY IEEE;
557 USE IEEE.STD_LOGIC_1164.ALL;
558 USE IEEE.STD_LOGIC_ARITH.ALL;
559
560 ENTITY ANALYZE_RESULT IS
561     PORT(SF1,SF2,SF3: IN STD_LOGIC:= '0'; --input the result of system
562           CF1,CF2,CF3: IN STD_LOGIC:= '0'; --input correct result
563           Clk: IN STD_LOGIC:= '0'); --clock input
564 END ENTITY ANALYZE_RESULT;
565
566 ARCHITECTURE ANALYZE OF ANALYZE_RESULT IS
567 BEGIN
568     PROCESS --to ensure that the system output is equal to the theoretical output
569     BEGIN
570         assert ((SF1 = CF1) AND (SF2 = CF2) AND (SF3 = CF3)) --if the system output is not equal to the theoretical output print an error
571         report "The obtained results do not accord with the theoretical result !!";
572         severity ERROR;
573         WAIT UNTIL rising_edge(Clk);
574     END PROCESS;
575 END ARCHITECTURE ANALYZE;
```

7.12. Code of Verification Stage 1 & Stage 2

```

578 -----
579 --           Verification circuit           --
580 -----
581 LIBRARY IEEE;
582 USE IEEE.STD_LOGIC_1164.ALL;
583 USE IEEE.STD_LOGIC_ARITH.ALL;
584
585 ENTITY VERIFICATION IS
586 END ENTITY VERIFICATION;
587
588 -----
589 --           Verification Stage_1           --
590 -----
591 ARCHITECTURE VERIF_STAGE_1 OF VERIFICATION IS
592     SIGNAL A,B: STD_LOGIC_VECTOR(7 DOWNTO 0):="00000000";
593     SIGNAL SF1,SF2,SF3: STD_LOGIC:='0'; --input the result of system
594     SIGNAL CF1,CF2,CF3: STD_LOGIC:='0'; --input correct result
595     SIGNAL Clk: STD_LOGIC:='0';
596
597 BEGIN
598     Clk <= NOT CLK AFTER 133| NS;
599     V1: ENTITY WORK.TEST_GENERATOR(BEH_TEST_GENERATOR) PORT MAP(Clk , A , B , CF1 , CF2 , CF3);
600     V2: ENTITY WORK.STAGE_1(STRUCT_STAGE_1) PORT MAP(A , B , SF1 , SF2 , SF3);
601     V3: ENTITY WORK.ANALYZE_RESULT(ANALYZE) PORT MAP(SF1 , SF2 , SF3 , CF1 , CF2 , CF3 , Clk);
602 END ARCHITECTURE VERIF_STAGE_1;
603
604 -----
605 --           Verification Stage_2           --
606 -----
607 ARCHITECTURE VERIF_STAGE_2 OF VERIFICATION IS
608     SIGNAL A,B: STD_LOGIC_VECTOR(7 DOWNTO 0):="00000000";
609     SIGNAL SF1,SF2,SF3: STD_LOGIC:='0'; --input the result of system
610     SIGNAL CF1,CF2,CF3: STD_LOGIC:='0'; --input correct result
611     SIGNAL Clk: STD_LOGIC:='0';
612
613 BEGIN
614     Clk <= NOT CLK AFTER 25 NS;
615     V1: ENTITY WORK.TEST_GENERATOR(BEH_TEST_GENERATOR) PORT MAP(Clk , A , B , CF1 , CF2 , CF3);
616     V2: ENTITY WORK.STAGE_2(STRUCT_STAGE_2) PORT MAP(A , B , SF1 , SF2 , SF3);
617     V3: ENTITY WORK.ANALYZE_RESULT(ANALYZE) PORT MAP(SF1 , SF2 , SF3 , CF1 , CF2 , CF3 , Clk);
618 END ARCHITECTURE VERIF_STAGE_2;
619
620 -----
621
622 -----

```

7.13. Full Code with comments

```

-----
--           COURSE PROJECT           --
-----

--                                     Tariq Odeh                                     --
--                                     1190699                                       --
--                                     sec: 2                                         --
-----

-----Basic gates with delay-----

```

-- INVERTER GATE (1 PORT) --

LIBRARY IEEE;

USE IEEE.STD_LOGIC_1164.ALL;

ENTITY NOT_1P IS

 PORT(A: IN STD_LOGIC:= '0'; --1 bit Input

 F: OUT STD_LOGIC:= '0'); --1 bit Output

END ENTITY NOT_1P;

ARCHITECTURE STRUCT_NOT_1P OF NOT_1P IS

 BEGIN

 F <= NOT A AFTER 2 NS; --2 ns delay

END ARCHITECTURE STRUCT_NOT_1P;

-- NAND GATE (N-BIT) --

LIBRARY IEEE;

USE IEEE.STD_LOGIC_1164.ALL;

ENTITY NAND_NBIT IS

 GENERIC (N : POSITIVE := 2); --N bit Input

 PORT(A: IN STD_LOGIC_VECTOR (N-1 DOWNT0 0):= "00000000";

 F: OUT STD_LOGIC:= '0'); --1 bit Output

END ENTITY NAND_NBIT;

ARCHITECTURE STRUCT_NAND_NBIT OF NAND_NBIT IS

 SIGNAL TEMP : STD_LOGIC_VECTOR (N-1 DOWNT0 0);

```

BEGIN

    TEMP(0) <= A(0);

    FLOOP: FOR i IN 1 TO (N-1) GENERATE

        TEMP(i) <= TEMP(i-1) AND A(i);

    END GENERATE FLOOP;

    F <= NOT(TEMP(N-1)) AFTER 5 NS;    --NAND = NOT(AND)
END ARCHITECTURE STRUCT_NAND_NBIT;    --5 ns delay

```

```

-----
--      NAND GATE (2 PORTS)      --
-----

```

```

LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;

```

```

ENTITY NAND_2P IS

    PORT(A,B: IN STD_LOGIC:= '0'; --2 bit Input

        F: OUT STD_LOGIC:= '0');    --1 bit Output

END ENTITY NAND_2P;

```

```

ARCHITECTURE STRUCT_NAND_2P OF NAND_2P IS

    BEGIN

        F <= A NAND B AFTER 5 NS;    --5 ns delay

        -- F <= NOT(A AND B) AFTER 5 NS;

END ARCHITECTURE STRUCT_NAND_2P;

```

```

-----
--      NOR GATE (N-BIT)      --
-----

```

```

LIBRARY IEEE;

```



```
USE IEEE.STD_LOGIC_1164.ALL;
```

```
ENTITY NOR_NBIT IS
```

```
    GENERIC ( N : POSITIVE := 2); --N bit Input
```

```
    PORT(A: IN STD_LOGIC_VECTOR (N-1 DOWNT0 0):= "00000000");
```

```
        F: OUT STD_LOGIC:= '0');                --1 bit Output
```

```
END ENTITY NOR_NBIT;
```

```
ARCHITECTURE STRUCT_NOR_NBIT OF NOR_NBIT IS
```

```
    SIGNAL TEMP : STD_LOGIC_VECTOR (N-1 DOWNT0 0);
```

```
    BEGIN
```

```
        TEMP(0) <= A(0);
```

```
        FLOOP: FOR i IN 1 TO (N-1) GENERATE
```

```
            TEMP(i) <= TEMP(i-1) OR A(i);
```

```
        END GENERATE FLOOP;
```

```
        F <= NOT(TEMP(N-1)) AFTER 5 NS;    --NOR = NOT(OR)
```

```
END ARCHITECTURE STRUCT_NOR_NBIT;        --5 ns delay
```

```
-----  
--      NOR GATE (2 PORTS)      --  
-----
```

```
LIBRARY IEEE;
```

```
USE IEEE.STD_LOGIC_1164.ALL;
```

```
ENTITY NOR_2P IS
```

```
    PORT(A,B: IN STD_LOGIC:= '0'; --2 bit Input
```

```
        F: OUT STD_LOGIC:= '0');    --1 bit Output
```

```
END ENTITY NOR_2P;
```

```
ARCHITECTURE STRUCT_NOR_2P OF NOR_2P IS
```

```

BEGIN

    F <= A NOR B AFTER 5 NS;      --5 ns delay

    -- F <= NOT(A OR B) AFTER 5 NS;

END ARCHITECTURE STRUCT_NOR_2P;


-----

--      AND GATE (N-BIT)      --
-----

LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;

ENTITY AND_NBIT IS
    GENERIC ( N : POSITIVE := 2);    --N bit Input
    PORT(A: IN STD_LOGIC_VECTOR (N-1 DOWNT0 0):= "00000000";
          F: OUT STD_LOGIC:= '0');    --1 bit Output
END ENTITY AND_NBIT;

ARCHITECTURE STRUCT_AND_NBIT OF AND_NBIT IS
    SIGNAL TEMP : STD_LOGIC_VECTOR (N-1 DOWNT0 0);

    BEGIN

        TEMP(0) <= A(0);

        FLOOP: FOR i IN 1 TO (N-1) GENERATE
            TEMP(i) <= TEMP(i-1) AND A(i);
        END GENERATE FLOOP;

        F <= TEMP(N-1) AFTER 7 NS;    --7 ns delay

    END ARCHITECTURE STRUCT_AND_NBIT;


-----

--      AND GATE (2 PORTS)      --
-----

```

```

-----

LIBRARY IEEE;

USE IEEE.STD_LOGIC_1164.ALL;

ENTITY AND_2P IS

    PORT(A,B: IN STD_LOGIC:= '0';  --2 bit Input

          F: OUT STD_LOGIC:= '0');    --1 bit Output

END ENTITY AND_2P;

```

```

ARCHITECTURE STRUCT_AND_2P OF AND_2P IS

    BEGIN

        F <= A AND B AFTER 7 NS;      --7 ns delay

END ARCHITECTURE STRUCT_AND_2P;

```

```

-----

--          OR GATE (N-BIT)          --

-----

```

```

LIBRARY IEEE;

USE IEEE.STD_LOGIC_1164.ALL;

ENTITY OR_NBIT IS

    GENERIC ( N : POSITIVE := 2); --N bit Input

    PORT(A: IN STD_LOGIC_VECTOR (N-1 DOWNT0 0):= "00000000";

          F: OUT STD_LOGIC:= '0');      --1 bit Output

END ENTITY OR_NBIT;

```

```

ARCHITECTURE STRUCT_OR_NBIT OF OR_NBIT IS

    SIGNAL TEMP : STD_LOGIC_VECTOR (N-1 DOWNT0 0);

    BEGIN

        TEMP(0) <= A(0);

```

```

        FLOOP: FOR i IN 1 TO (N-1) GENERATE
            TEMP(i) <= TEMP(i-1) OR A(i);
        END GENERATE FLOOP;

        F <= TEMP(N-1) AFTER 7 NS;  --7 ns delay
END ARCHITECTURE STRUCT_OR_NBIT;

-----

--      OR GATE (2 PORTS)      --
-----

LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;

ENTITY OR_2P IS
    PORT(A,B: IN STD_LOGIC:= '0';  --2 bit Input
          F: OUT STD_LOGIC:= '0');  --1 bit Output
END ENTITY OR_2P;

ARCHITECTURE STRUCT_OR_2P OF OR_2P IS
    BEGIN
        F <= A OR B AFTER 7 NS;      --7 ns delay
END ARCHITECTURE STRUCT_OR_2P;

-----

--      XNOR GATE (2 PORTS)    --
-----

LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;

ENTITY XNOR_2P IS
    PORT(A,B: IN STD_LOGIC:= '0';  --2 bit Input
          F: OUT STD_LOGIC:= '0');  --1 bit Output

```

```
END ENTITY XNOR_2P;
```

```
ARCHITECTURE STRUCT_XNOR_2P OF XNOR_2P IS
```

```
BEGIN
```

```
    F <= A XNOR B AFTER 9 NS;    --9 ns delay
```

```
END ARCHITECTURE STRUCT_XNOR_2P;
```

```
-----  
--      XOR GATE (2 PORTS)      --  
-----
```

```
LIBRARY IEEE;
```

```
USE IEEE.STD_LOGIC_1164.ALL;
```

```
ENTITY XOR_2P IS
```

```
    PORT(A,B: IN STD_LOGIC:= '0'; --2 bit Input
```

```
          F: OUT STD_LOGIC:= '0');    --1 bit Output
```

```
END ENTITY XOR_2P;
```

```
ARCHITECTURE STRUCT_XOR_2P OF XOR_2P IS
```

```
BEGIN
```

```
    F <= A XOR B AFTER 12 NS;    --12 ns delay
```

```
END ARCHITECTURE STRUCT_XOR_2P;
```

```
-----  
--      Half Adder      --  
-----
```

```
LIBRARY IEEE;
```

```
USE IEEE.STD_LOGIC_1164.ALL;
```

ENTITY HA IS

```
    PORT(A,B: IN STD_LOGIC:= '0';           --Input
          Sum,Cout: OUT STD_LOGIC:= '0');    --Output
```

END ENTITY HA;

ARCHITECTURE STRUCT_HA OF HA IS

```
    SIGNAL X : STD_LOGIC_VECTOR (1 DOWNT0 0):= "00";

    BEGIN

        X <= A & B;

        H1:    ENTITY WORK.XOR_2P(STRUCT_XOR_2P) PORT MAP (A,B,Sum);
        --Sum = A XOR B

        H2:    ENTITY WORK.AND_NBIT(STRUCT_AND_NBIT) GENERIC MAP(2) PORT
MAP (X,Cout); --Cout = A AND B

    END ARCHITECTURE STRUCT_HA;
```

-- Full Adder --

LIBRARY IEEE;

USE IEEE.STD_LOGIC_1164.ALL;

ENTITY FAD IS

```
    PORT(A,B,Cin: IN STD_LOGIC:= '0';
          Sum,Cout: OUT STD_LOGIC:= '0');
```

END ENTITY FAD;

ARCHITECTURE STRUCT_FAD OF FAD IS

```
    SIGNAL N1,N2,N3,N4,N5,N6,N7: STD_LOGIC := '0';
```

BEGIN

--First way to implement Full Adder Using XOR,AND,OR

gates

```

--F1: ENTITY WORK.XOR_2P(STRUCT_XOR_2P) PORT MAP(A,B,N1);
--SUM = A XOR B XOR Cin

--F2: ENTITY WORK.XOR_2P(STRUCT_XOR_2P) PORT MAP(N1,Cin,Sum); --
Cout = Cin.(A XOR B) + A.B

--F3: ENTITY WORK.AND_2P(STRUCT_AND_2P) PORT MAP(A,B,N2);
--F4: ENTITY WORK.AND_2P(STRUCT_AND_2P) PORT MAP(N1,Cin,N3);
--F5: ENTITY WORK.OR_2P(STRUCT_OR_2P) PORT MAP(N2,N3,Cout);

```

--Second way to implement Full Adder Using Half Adder

```

--F1: ENTITY WORK.HA(STRUCT_HA) PORT MAP(A,B,N1,N2);
--F2: ENTITY WORK.HA(STRUCT_HA) PORT MAP(N1,Cin,Sum,N3);
--F3: ENTITY WORK.OR_2P(STRUCT_OR_2P) PORT MAP(N2,N3,Cout);

```

--Third way to implement Full Adder Using NAND gate

(faster)

```

F1: ENTITY WORK.NAND_2P(STRUCT_NAND_2P) PORT MAP(A,B,N1);
F2: ENTITY WORK.NAND_2P(STRUCT_NAND_2P) PORT MAP(N1,A,N2);
F3: ENTITY WORK.NAND_2P(STRUCT_NAND_2P) PORT MAP(N1,B,N3);
F4: ENTITY WORK.NAND_2P(STRUCT_NAND_2P) PORT MAP(N2,N3,N4);
F5: ENTITY WORK.NAND_2P(STRUCT_NAND_2P) PORT MAP(N4,Cin,N5);
F6: ENTITY WORK.NAND_2P(STRUCT_NAND_2P) PORT MAP(N5,N1,Cout);
F7: ENTITY WORK.NAND_2P(STRUCT_NAND_2P) PORT MAP(N5,Cin,N6);
F8: ENTITY WORK.NAND_2P(STRUCT_NAND_2P) PORT MAP(N5,N4,N7);
F9: ENTITY WORK.NAND_2P(STRUCT_NAND_2P) PORT MAP(N6,N7,Sum);

```

```

END ARCHITECTURE STRUCT_FAD;

```

```

-----
--      n-Bit Ripple Adder/subtractor      --
-----

```

```

LIBRARY IEEE;

```

```
USE IEEE.STD_LOGIC_1164.ALL;
```

```
ENTITY NBIT_ADDER IS
```

```
    GENERIC ( N : POSITIVE :=8);
```

```
    PORT(A,B: IN STD_LOGIC_VECTOR (N-1 DOWNT0 0):= "00000000";
```

```
        Cin: IN STD_LOGIC :='1';                --Set Cin = 1 to find 2's  
complement for B
```

```
        Sum: OUT STD_LOGIC_VECTOR(N-1 DOWNT0 0):= "00000000";
```

```
        Cout, OV: OUT STD_LOGIC:= '0');        --OV (overflow)
```

```
END ENTITY NBIT_ADDER;
```

```
ARCHITECTURE STRUCT_RIPPLE OF NBIT_ADDER IS
```

```
    SIGNAL CARRY : STD_LOGIC_VECTOR (N DOWNT0 0):= "000000000";
```

```
    SIGNAL X :STD_LOGIC_VECTOR (N-1 DOWNT0 0):= "00000000"; --to save 2's  
complement of B
```

```
    BEGIN
```

```
        CARRY(0) <= Cin;
```

```
        Cout <= CARRY(N);
```

```
        R1: ENTITY WORK.XOR_2P(STRUCT_XOR_2P) PORT MAP (CARRY(N),CARRY(N-  
1),OV);
```

```
        FLOOP: FOR i IN 0 TO (N-1) GENERATE        --Loop to generate ripple  
Adder/subtractor
```

```
            R2: ENTITY WORK.XOR_2P(STRUCT_XOR_2P) PORT MAP (B(i),Cin,X(i));  
--if Cin = 0 then ripple Adder work, if Cin = 1 ripple subtractor work
```

```
            R3: ENTITY WORK.FAD(STRUCT_FAD) PORT MAP  
(A(i),X(i),CARRY(i),Sum(i),CARRY(i+1));
```

```
        END GENERATE FLOOP;
```

```
END ARCHITECTURE STRUCT_RIPPLE;
```

```
-----  
----          n-Bit Comparator          --  
-----
```



```

LIBRARY IEEE;

USE IEEE.STD_LOGIC_1164.ALL;

ENTITY NBIT_COMPARATOR IS
    GENERIC ( N : POSITIVE :=8);
    PORT(A,B: IN STD_LOGIC_VECTOR (N-1 DOWNT0 0):= "00000000";    --Input
          F1,F2,F3: OUT STD_LOGIC:= '0';    --Output: F1(A=B), F2(A>B), and
F3 (A<B).
END ENTITY NBIT_COMPARATOR;

ARCHITECTURE STRUCT_NBIT_COMPARATOR OF NBIT_COMPARATOR IS
    SIGNAL SUM : STD_LOGIC_VECTOR (N-1 DOWNT0 0):= "00000000";

    SIGNAL Cout,X,S : STD_LOGIC:= '0';    --X to check overflow, S to check if sum
equal zero

    SIGNAL NC,NS,NX: STD_LOGIC:= '0'; --NC (not Cout) ,NS (not S(N-1)),NX (not Overflow)

    SIGNAL FF1,FF2,FF3: STD_LOGIC:= '0'; --to save output of F1,F2,F3 if there is overflow

    SIGNAL FFF1,FFF2,FFF3: STD_LOGIC:= '0';--to save output of F1,F2,F3 if there is not
overflow

    SIGNAL A1,A2,B1,B2: STD_LOGIC:= '0';

    BEGIN

        P1: ENTITY WORK.NBIT_ADDER(STRUCT_RIPPLE) GENERIC MAP(N) PORT
MAP(A,B,'1',SUM,Cout,X);    --ripple subtractor    (the output of overflow save in X)

        P3: ENTITY WORK.OR_NBIT(STRUCT_OR_NBIT) GENERIC MAP(N) PORT
MAP(SUM,S);    --check if sum equal zero

        P4: ENTITY WORK.NOT_1P(STRUCT_NOT_1P)PORT MAP(Cout,NC);
    --NC (not Cout)

        P5: ENTITY WORK.NOT_1P(STRUCT_NOT_1P)PORT MAP(SUM(N-1),NS);
    --NS (not S(N-1))

        P6: ENTITY WORK.NOT_1P(STRUCT_NOT_1P)PORT MAP(X,NX);
    --NX (not Overflow)

        X1: ENTITY WORK.NOR_2P(STRUCT_NOR_2P) PORT MAP (Cout,S,A1);    --
find the value of F1,F2,F3 if there is overflow

```

```

X2: ENTITY WORK.AND_2P(STRUCT_AND_2P) PORT MAP (NC,S,A2);
X3: ENTITY WORK.AND_2P(STRUCT_AND_2P) PORT MAP (X,A1,FF1);
X4: ENTITY WORK.AND_2P(STRUCT_AND_2P) PORT MAP (X,A2,FF2);
X5: ENTITY WORK.AND_2P(STRUCT_AND_2P) PORT MAP (X,Cout,FF3);

Y1: ENTITY WORK.NOR_2P(STRUCT_NOR_2P) PORT MAP (SUM(N-1),S,B1);
--find the value of F1,F2,F3 if there is not overflow
Y2: ENTITY WORK.AND_2P(STRUCT_AND_2P) PORT MAP (NS,S,B2);
Y3: ENTITY WORK.AND_2P(STRUCT_AND_2P) PORT MAP (NX,B1,FFF1);
Y4: ENTITY WORK.AND_2P(STRUCT_AND_2P) PORT MAP (NX,B2,FFF2);
Y5: ENTITY WORK.AND_2P(STRUCT_AND_2P) PORT MAP (NX,SUM(N-1),FFF3);

Z1: ENTITY WORK.OR_2P(STRUCT_OR_2P) PORT MAP(FF1,FFF1,F1);      --
final value of F1,F2,F3
Z2: ENTITY WORK.OR_2P(STRUCT_OR_2P) PORT MAP(FF2,FFF2,F2);
Z3: ENTITY WORK.OR_2P(STRUCT_OR_2P) PORT MAP(FF3,FFF3,F3);

END ARCHITECTURE STRUCT_NBIT_COMPARATOR;

-----

----  Stage_1 with ripple adder/subtractor  --
-----

LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;

ENTITY STAGE_1 IS
    PORT(A,B: IN STD_LOGIC_VECTOR (7 DOWNT0 0):= "00000000";      --8-bit input
          F1,F2,F3: OUT STD_LOGIC:='0');
    --Output: F1(A=B), F2(A>B), and F3 (A<B).
END ENTITY STAGE_1;

```

ARCHITECTURE STRUCT_STAGE_1 OF STAGE_1 IS

BEGIN

S1: ENTITY WORK.NBIT_COMPARATOR(STRUCT_NBIT_COMPARATOR) GENERIC
MAP(8) PORT MAP(A,B,F1,F2,F3);

END ARCHITECTURE STRUCT_STAGE_1;

--

=====

--

=====

-- 1-Bit Magnitude comparator --

LIBRARY IEEE;

USE IEEE.STD_LOGIC_1164.ALL;

ENTITY MAGNCOMP_1BIT IS

PORT(A,B: IN STD_LOGIC:= '0'; --1-Bit input

F1,F2,F3: OUT STD_LOGIC:= '0'); --Output: F1(A=B), F2(A>B), and F3 (A<B)

END ENTITY MAGNCOMP_1BIT;

ARCHITECTURE STRUCT_MAGNCOMP_1BIT OF MAGNCOMP_1BIT IS

SIGNAL NA,NB : STD_LOGIC:= '0'; --NA(not A) , NB(not B)

BEGIN

M1: ENTITY WORK.XNOR_2P(STRUCT_XNOR_2P)PORT MAP(A,B,F1);

M2: ENTITY WORK.NOT_1P(STRUCT_NOT_1P)PORT MAP(B,NB);

M3: ENTITY WORK.AND_2P(STRUCT_AND_2P)PORT MAP(A,NB,F2);

M4: ENTITY WORK.NOT_1P(STRUCT_NOT_1P)PORT MAP(A,NA);

M5: ENTITY WORK.AND_2P(STRUCT_AND_2P)PORT MAP(NA,B,F3);

```
END ARCHITECTURE STRUCT_MAGNCOMP_1BIT;
```

```
-----  
--      4-Bit Magnitude comparator      --  
-----
```

```
LIBRARY IEEE;
```

```
USE IEEE.STD_LOGIC_1164.ALL;
```

```
ENTITY MAGNCOMP_4BIT IS
```

```
    PORT(A,B: IN STD_LOGIC_VECTOR (3 DOWNT0 0):= "0000";    --4-Bit input  
          F1,F2,F3: OUT STD_LOGIC:= '0');                    --Output: F1(A=B), F2(A>B), and  
    F3 (A<B).
```

```
END ENTITY MAGNCOMP_4BIT;
```

```
ARCHITECTURE STRUCT_MAGNCOMP_4BIT OF MAGNCOMP_4BIT IS
```

```
    SIGNAL E,G,L :STD_LOGIC_VECTOR (3 DOWNT0 0):= "0000"; --E(equal)A=B,  
    G(greater)A>B, L(less)A<B
```

```
    SIGNAL GT,LT :STD_LOGIC_VECTOR (3 DOWNT0 0):= "0000";
```

```
    SIGNAL LL1,GG1 :STD_LOGIC_VECTOR (1 DOWNT0 0):= "00";
```

```
    SIGNAL LL2,GG2 :STD_LOGIC_VECTOR (2 DOWNT0 0):= "000";
```

```
    SIGNAL LL3,GG3 :STD_LOGIC_VECTOR (3 DOWNT0 0):= "0000";
```

```
    SIGNAL X1,X2,X3,X4,X5,X6 :STD_LOGIC := '0';
```

```
BEGIN
```

```
    FLOOP1: FOR i IN 0 TO (3) GENERATE    --loop to compare 4 bit by using 1-Bit  
    Magnitude comparator
```

```
        M1: ENTITY WORK.MAGNCOMP_1BIT(STRUCT_MAGNCOMP_1BIT)  
    PORT MAP (A(i),B(i),E(i),G(i),L(i));
```

```
    END GENERATE FLOOP1;
```

```
    LL1 <= L(2)&E(3); --To find out the possibilities for greater or less
```

```
    GG1 <= G(2)&E(3);
```

```

LL2 <= L(1)&E(3)&E(2);

GG2 <= G(1)&E(3)&E(2);

LL3 <= L(0)&E(3)&E(2)&E(1);

GG3 <= G(0)&E(3)&E(2)&E(1);


M2: ENTITY WORK.AND_NBIT(STRUCT_AND_NBIT) GENERIC MAP(2) PORT
MAP(LL1,X1);

M3: ENTITY WORK.AND_NBIT(STRUCT_AND_NBIT) GENERIC MAP(2) PORT
MAP(GG1,X2);

M4: ENTITY WORK.AND_NBIT(STRUCT_AND_NBIT) GENERIC MAP(3) PORT
MAP(LL2,X3);

M5: ENTITY WORK.AND_NBIT(STRUCT_AND_NBIT) GENERIC MAP(3) PORT
MAP(GG2,X4);

M6: ENTITY WORK.AND_NBIT(STRUCT_AND_NBIT) GENERIC MAP(4) PORT
MAP(LL3,X5);

M7: ENTITY WORK.AND_NBIT(STRUCT_AND_NBIT) GENERIC MAP(4) PORT
MAP(GG3,X6);


GT <= G(3)&X2&X4&X6; --to check if greater or less

LT <= L(3)&X1&X3&X5;


M8: ENTITY WORK.AND_NBIT(STRUCT_AND_NBIT) GENERIC MAP(4) PORT
MAP(E,F1);

M9: ENTITY WORK.OR_NBIT(STRUCT_OR_NBIT) GENERIC MAP(4) PORT
MAP(GT,F2);

M10: ENTITY WORK.OR_NBIT(STRUCT_OR_NBIT) GENERIC MAP(4) PORT
MAP(LT,F3);

END ARCHITECTURE STRUCT_MAGNCOMP_4BIT;

```

```

-----
--      8-Bit Magnitude comparator      --
-----

```

```

LIBRARY IEEE;

```

```
USE IEEE.STD_LOGIC_1164.ALL;
```

```
ENTITY MAGNCOMP_8BIT IS
```

```
    PORT(A,B: IN STD_LOGIC_VECTOR (7 DOWNT0 0):= "00000000";          --8-Bit input
          F1,F2,F3: OUT STD_LOGIC:= '0');          --Output: F1(A=B), F2(A>B), and
F3 (A<B).
END ENTITY MAGNCOMP_8BIT;
```

```
ARCHITECTURE STRUCT_MAGNCOMP_8BIT OF MAGNCOMP_8BIT IS
```

```
    SIGNAL T1,T2,T3,T4 :STD_LOGIC_VECTOR (3 DOWNT0 0):= "0000"; --To save A and B
    SIGNAL E1,G1,L1 :STD_LOGIC:= '0'; --To save the output of the first 4-Bit Magnitude
comparator
    SIGNAL E2,G2,L2 :STD_LOGIC:= '0'; --To save the output of the second 4-Bit Magnitude
comparator
    SIGNAL GG,LL :STD_LOGIC:= '0';
```

```
BEGIN
```

```
    T1 <= A(3)&A(2)&A(1)&A(0);
    T2 <= B(3)&B(2)&B(1)&B(0);
    T3 <= A(7)&A(6)&A(5)&A(4);
    T4 <= B(7)&B(6)&B(5)&B(4);
```

```
    M1: ENTITY WORK.MAGNCOMP_4BIT(STRUCT_MAGNCOMP_4BIT) PORT MAP
(T1,T2,E1,G1,L1);
```

```
    M2: ENTITY WORK.MAGNCOMP_4BIT(STRUCT_MAGNCOMP_4BIT) PORT MAP
(T3,T4,E2,G2,L2);
```

```
    M3: ENTITY WORK.AND_2P(STRUCT_AND_2P)PORT MAP(E2,G1,GG); --To find
out the possibilities for greater or less
```

```
    M4: ENTITY WORK.AND_2P(STRUCT_AND_2P)PORT MAP(E2,L1,LL);
```

```
    M5: ENTITY WORK.AND_2P(STRUCT_AND_2P)PORT MAP(E1,E2,F1);
```

```
    M6: ENTITY WORK.OR_2P(STRUCT_OR_2P)PORT MAP(G2,GG,F2);
```

```
    M7: ENTITY WORK.OR_2P(STRUCT_OR_2P)PORT MAP(L2,LL,F3);
```

```
END ARCHITECTURE STRUCT_MAGNCOMP_8BIT;
```

```
-----  
----   Stage_2 with Magnitude comparator   --  
-----
```

```
LIBRARY IEEE;
```

```
USE IEEE.STD_LOGIC_1164.ALL;
```

```
ENTITY STAGE_2 IS
```

```
    PORT(A,B: IN STD_LOGIC_VECTOR (7 DOWNT0 0):= "00000000";      --8-bit input
```

```
          F1,F2,F3: OUT STD_LOGIC:= '0');
```

```
    --Output: F1(A=B), F2(A>B), and F3 (A<B).
```

```
END ENTITY STAGE_2;
```

```
ARCHITECTURE STRUCT_STAGE_2 OF STAGE_2 IS
```

```
    SIGNAL X, FF2,FF3 : STD_LOGIC:= '0';
```

```
    BEGIN
```

```
        S1: ENTITY WORK.MAGNCOMP_8BIT(STRUCT_MAGNCOMP_8BIT) PORT  
MAP(A,B,F1,FF2,FF3);
```

```
        S2: ENTITY WORK.XOR_2P(STRUCT_XOR_2P)PORT MAP(A(7),B(7),X);    --To  
check sign bit
```

```
        S3: ENTITY WORK.XOR_2P(STRUCT_XOR_2P)PORT MAP(X,FF2,F2);    --To get a  
correct answer
```

```
        S4: ENTITY WORK.XOR_2P(STRUCT_XOR_2P)PORT MAP(X,FF3,F3);
```

```
END ARCHITECTURE STRUCT_STAGE_2;
```

```
--  
=====
```

```
=====
```

```

--
=====
=====

-----
Test Generator      --
-----

LIBRARY IEEE;

USE IEEE.STD_LOGIC_1164.ALL;

USE IEEE.STD_LOGIC_SIGNED.ALL;

USE IEEE.STD_LOGIC_ARITH.ALL;

ENTITY TEST_GENERATOR IS

    PORT(Clk: IN STD_LOGIC:= '0';
          --clock input

          A,B: OUT STD_LOGIC_VECTOR(7 DOWNT0 0):= "00000000";    --8 bit output:

          F1,F2,F3: OUT STD_LOGIC:= '0');                        --
    Output: F1(A=B), F2(A>B), and F3 (A<B)

END ENTITY TEST_GENERATOR;

ARCHITECTURE BEH_TEST_GENERATOR OF TEST_GENERATOR IS

    SIGNAL IN1,IN2: STD_LOGIC_VECTOR(7 DOWNT0 0):= "00000000";

    BEGIN

        A <= IN1;          --set the value of IN1 in A to send it to comparator

        B <= IN2;          --set the value of IN2 in B to send it to comparator

        PROCESS            --changes the values of IN1 and IN2 also (A and B) when the
clock positive edge

            BEGIN

                FOR i IN -128 TO 127 LOOP    --to go through all possible values

                    FOR j IN -128 TO 127 LOOP

                        IN1(7 DOWNT0 0) <=
CONV_STD_LOGIC_VECTOR(i,8);    --conv from integer to STD_LOGIC

```



```

                                IN2(7 DOWNT0 0) <=
CONV_STD_LOGIC_VECTOR(j,8);    --conv from integer to STD_LOGIC

                                WAIT UNTIL rising_edge(Clk);

                                END LOOP;

                                END LOOP;

                                WAIT;

                                END PROCESS;

                                PROCESS (IN1,IN2)    --implement the system using behavioural logic
                                BEGIN
                                    IF(IN1 > IN2) THEN
                                        F1 <= '0' ;
                                        F2 <= '1' ;
                                        F3 <= '0' ;
                                    ELSIF (IN1 < IN2) THEN
                                        F1 <= '0' ;
                                        F2 <= '0' ;
                                        F3 <= '1' ;
                                    ELSE
                                        F1 <= '1' ;
                                        F2 <= '0' ;
                                        F3 <= '0' ;
                                    END IF;
                                END PROCESS;

                                END ARCHITECTURE BEH_TEST_GENERATOR;

```

```

-----
--           Analyze           --
-----

```

```

LIBRARY IEEE;

```

```

USE IEEE.STD_LOGIC_1164.ALL;

USE IEEE.STD_LOGIC_ARITH.ALL;


ENTITY ANALYZE_RESULT IS
    PORT(SF1,SF2,SF3: IN STD_LOGIC:='0'; --input the result of system
          CF1,CF2,CF3: IN STD_LOGIC:='0'; --input correct result
          Clk: IN STD_LOGIC:='0');      --clock input
END ENTITY ANALYZE_RESULT;


ARCHITECTURE ANALYZE OF ANALYZE_RESULT IS
    BEGIN
        PROCESS                                --to ensure that the system output is equal to
the theoretical output
            BEGIN
                assert ((SF1 = CF1) AND (SF2 = CF2) AND (SF3 = CF3))    --if the
system output is not equal to the theoretical output print an error
                report "The obtained results do not accord with the theoretical
result !!"
                severity ERROR;
                WAIT UNTIL rising_edge(Clk);
            END PROCESS;
END ARCHITECTURE ANALYZE;


-----
--      Verification circuit      --
-----

LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;
USE IEEE.STD_LOGIC_ARITH.ALL;


ENTITY VERIFICATION IS

```

END ENTITY VERIFICATION;

-- Verification Stage_1 --

ARCHITECTURE VERIF_STAGE_1 OF VERIFICATION IS

SIGNAL A,B: STD_LOGIC_VECTOR(7 DOWNTO 0):="00000000";

SIGNAL SF1,SF2,SF3: STD_LOGIC:='0'; --input the result of system

SIGNAL CF1,CF2,CF3: STD_LOGIC:='0'; --input correct result

SIGNAL Clk: STD_LOGIC:='0';

BEGIN

Clk <= NOT CLK AFTER 133 NS;

V1: ENTITY WORK.TEST_GENERATOR(BEH_TEST_GENERATOR) PORT MAP(Clk , A
, B , CF1 , CF2 , CF3);

V2: ENTITY WORK.STAGE_1(STRUCT_STAGE_1) PORT MAP(A , B , SF1 , SF2 ,
SF3);

V3: ENTITY WORK.ANALYZE_RESULT(ANALYZE) PORT MAP(SF1 , SF2 , SF3 , CF1 ,
CF2 , CF3 , Clk);

END ARCHITECTURE VERIF_STAGE_1;

-- Verification Stage_2 --

ARCHITECTURE VERIF_STAGE_2 OF VERIFICATION IS

SIGNAL A,B: STD_LOGIC_VECTOR(7 DOWNTO 0):="00000000";

SIGNAL SF1,SF2,SF3: STD_LOGIC:='0'; --input the result of system

SIGNAL CF1,CF2,CF3: STD_LOGIC:='0'; --input correct result

SIGNAL Clk: STD_LOGIC:='0';

```

BEGIN

    Clk <= NOT CLK AFTER 25 NS;

    V1: ENTITY WORK.TEST_GENERATOR(BEH_TEST_GENERATOR) PORT MAP(Clk , A
, B , CF1 , CF2 , CF3);

    V2: ENTITY WORK.STAGE_2(STRUCT_STAGE_2) PORT MAP(A , B , SF1 , SF2 ,
SF3);

    V3: ENTITY WORK.ANALYZE_RESULT(ANALYZE) PORT MAP(SF1 , SF2 , SF3 , CF1 ,
CF2 , CF3 , Clk);

END ARCHITECTURE VERIF_STAGE_2;

```

```

--
|=====
=====|
--|=====    D-flip-flop (1-bit) // D-flip-flop (n-bit) // n-Bit Carry Lookahead
=====|

```

```

--
|=====
=====|

```

```

-----
--      D-flip-flop (1-bit)      --
-----

```

```

--LIBRARY IEEE;

--USE IEEE.STD_LOGIC_1164.ALL;

--

--ENTITY DFF_1B IS

--      PORT(D,Clk,Reset: IN STD_LOGIC:= '0';          --Input

--              Q,NQ: OUT STD_LOGIC:= '0');              --Output

--END ENTITY DFF_1B;

--

--ARCHITECTURE STRUCT_DFF_1B OF DFF_1B IS

--  BEGIN

```

```

--          PROCESS(Reset,Clk)
--          BEGIN
--              IF (Reset = '1') THEN                      --Reset the dff when
reset is 1
--                  Q <= '0';
--                  NQ <= '0';
--              ELSE
--                  IF (rising_edge(Clk)) THEN  --On positive edge
--                      Q <= D ;
--                      NQ <= NOT D ;
--                  END IF;
--              END IF;
--          END PROCESS;
--END ARCHITECTURE STRUCT_DFF_1B;

```

```

-----
--      n-Bit (flip-flops/registers)      --
-----

```

```

--LIBRARY IEEE;
--USE IEEE.STD_LOGIC_1164.ALL;
--
--ENTITY NBIT_REGISTERS IS
--    GENERIC (N : POSITIVE := 16);
--    PORT (D: IN STD_LOGIC_vector(N-1 DOWNT0 0):= "00000000";      --Input
--          Clk,Reset: IN STD_LOGIC:= '0';
--          --Input
--          Q,NQ : OUT STD_LOGIC_vector(N-1 DOWNT0 0):= "00000000");  --
Output
--END ENTITY NBIT_REGISTERS;
--
--

```

```

--ARCHITECTURE STRUCT_NBIT_REGISTERS OF NBIT_REGISTERS IS

--      BEGIN

--          FLOOP : FOR i IN 0 TO (N-1) GENERATE                --Loop to generate n-bit
dff from 1-bit dff

--              G_DFF : ENTITY WORK.DFF_1B(STRUCT_DFF_1B) PORT
MAP(D(i),Clk,Reset,Q(i),NQ(i));

--          END GENERATE FLOOP;

--END ARCHITECTURE STRUCT_NBIT_REGISTERS;

```

```

-----
----      n-Bit Carry Lookahead      --
-----

```

```

--LIBRARY IEEE;

--USE IEEE.STD_LOGIC_1164.ALL;

--

--ENTITY LOOK_AHEAD IS      --look ahead adder/subtractor faster than ripple
adder/subtractor

--      GENERIC (N : POSITIVE := 8);

--      PORT (A,B: IN STD_LOGIC_VECTOR(N-1 DOWNT0 0):= "00000000";

--          Cin: IN  STD_LOGIC:= '0';

--          Sum: OUT STD_LOGIC_VECTOR(N-1 DOWNT0 0):= "00000000";

--          Cout: OUT STD_LOGIC:= '0');

--END ENTITY LOOK_AHEAD;

```

```

--
--ARCHITECTURE STRUCT_CARRY_LOOK_AHEAD OF LOOK_AHEAD IS

--      SIGNAL S,G,P: STD_LOGIC_VECTOR(N-1 DOWNT0 0):= "00000000";

--      SIGNAL C: STD_LOGIC_VECTOR(N-1 DOWNT0 1):= "00000000";

--      BEGIN

--          PROCESS (G,P,C)

--              BEGIN

--                  C(1) <= G(0) OR (P(0) AND Cin);

```

```

--      inst: FOR i IN 1 TO N-2 LOOP
--
--          C(i+1) <= G(i) OR (P(i) AND C(i));
--
--      END LOOP;
--
--      Cout <= G(N-1) OR (P(N-1) AND C(N-1));
--
--  END PROCESS;
--
--
--      FLOOP1: FOR i IN 0 TO (N-1) GENERATE
--
--          G1: ENTITY WORK.XOR_2P(STRUCT_XOR_2P) PORT
MAP(A(i),B(i),S(i));
--
--      END GENERATE FLOOP1;
--
--
--      FLOOP2: FOR i IN 0 TO (N-1) GENERATE
--
--          G2: ENTITY WORK.AND_2P(STRUCT_AND_2P) PORT
MAP(A(i),B(i),G(i));
--
--      END GENERATE FLOOP2;
--
--
--      FLOOP3: FOR i IN 0 TO (N-1) GENERATE
--
--          G3: ENTITY WORK.OR_2P(STRUCT_OR_2P) PORT
MAP(A(i),B(i),P(i));
--
--      END GENERATE FLOOP3;
--
--
--      G4: ENTITY WORK.XOR_2P(STRUCT_XOR_2P) PORT MAP(S(0),Cin,Sum(0));
--
--      FLOOP4: FOR i IN 1 TO (N-1) GENERATE
--
--          G5: ENTITY WORK.XOR_2P(STRUCT_XOR_2P) PORT
MAP(S(i),C(i),Sum(i));
--
--      END GENERATE FLOOP4;
--
--
--END ARCHITECTURE STRUCT_CARRY_LOOK_AHEAD;

```